


## AM - Demodulation

Prof. Hyunggon Park

Email: hyunggon.park@ewha.ac.kr  
Homepage: <http://mcnl.ewha.ac.kr>


Multimedia Communications and Networking Lab.  
Department of Electronic and Electrical Engineering  
Ewha Womans University

## AM Receiver

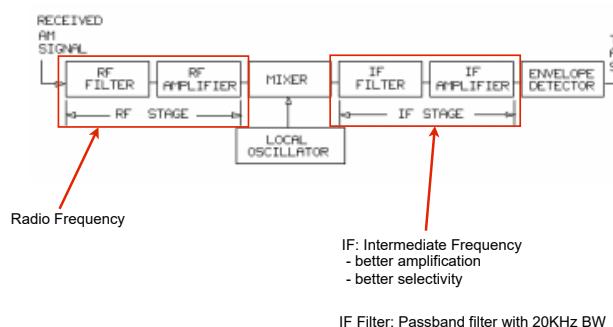

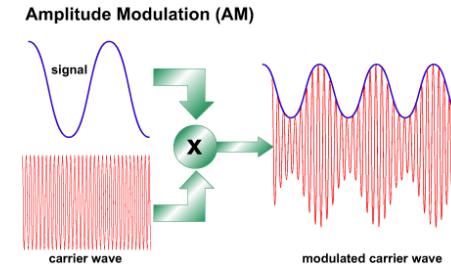
## Recall: AM

- **Amplitude** of carrier signal is varied in accordance to instantaneous amplitude of modulating signal




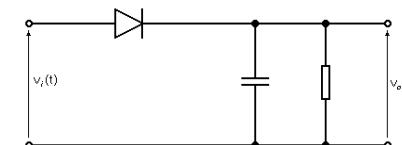
## Envelope Detector

- **Circuit**
    - Input: high-frequency signal
    - Output: "envelope" of the original signal.
  - **Capacitor**
    - stores up charge on the rising edge
    - releases it slowly through the resistor when the signal falls.




## MATLAB Example

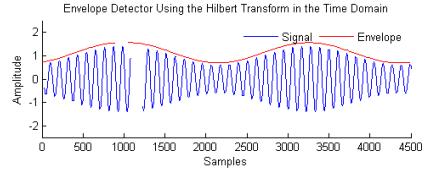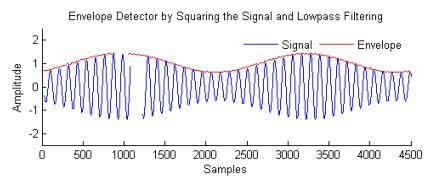


Try these examples by yourself!




## Animation

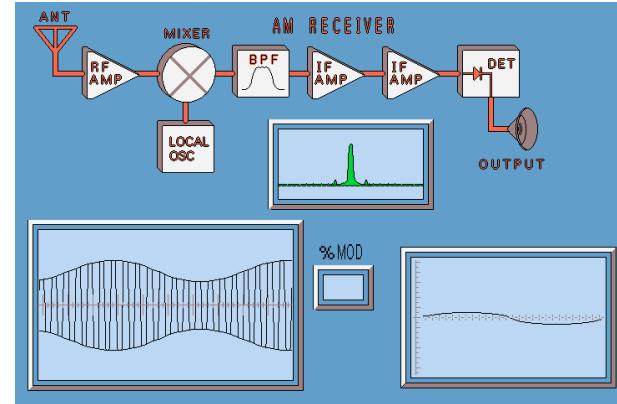

## Your experiments...

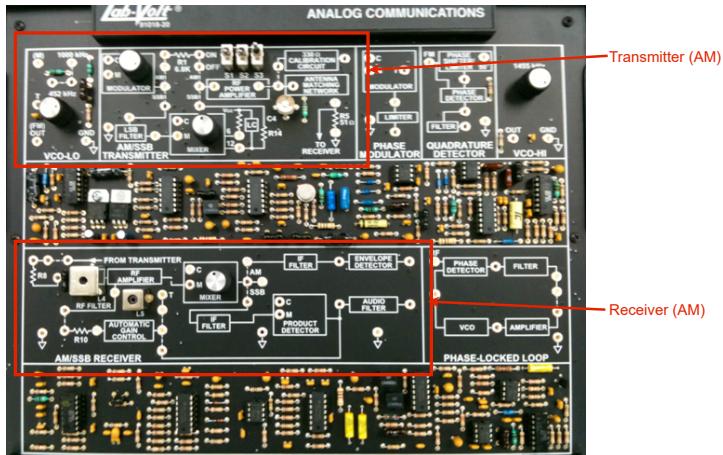


## AM Transmitter

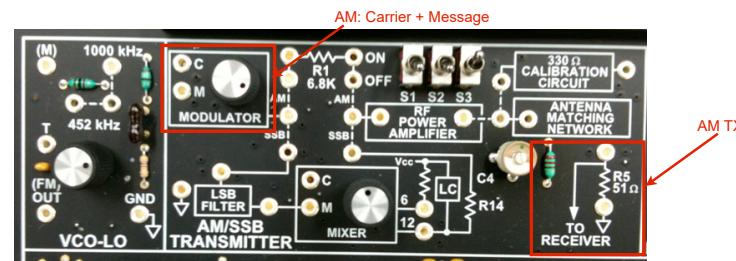

- You may play by changing
  - carrier frequency, modulation index, AM/SSB modes, etc.



## AM Receiver

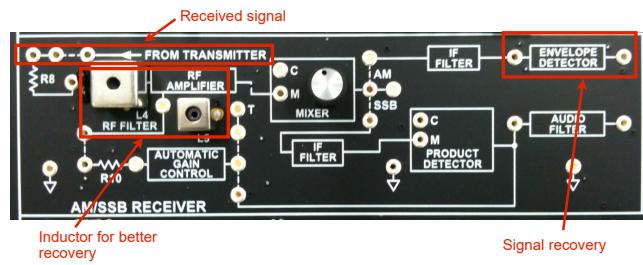


### Notes:

- Inductors are very **FRAGILE**: Please be **VERY** careful to handle them
- Sometimes, IF filter and envelope detector do not work well. In this case, try to see the very front input signal to these blocks – these are enough for your report (i.e., bypassing blocks that are not working)




## Illustrative results


### Demodulated Signals

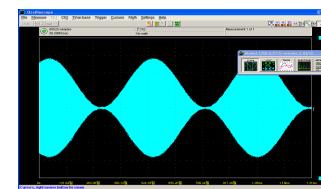

Received Signal

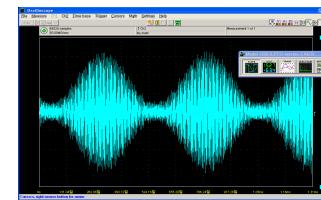

After RF

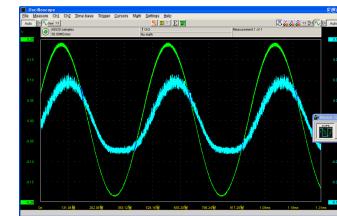

Recovered (Demodulated) signal

