



FM - Demodulation

Prof. Hyunggon Park

Email: hyunggon.park@ewha.ac.kr

Homepage: <http://mcnl.ewha.ac.kr>


Multimedia Communications and Networking Lab.
Department of Electronic and Electrical Engineering
Ewha Womans University

Recall: FM Demodulation

- AM demodulators:
 - cannot be used due to the constant amplitude of FM signals
- FM dedicated demodulator
 - Phase detector
 - The Foster-Seeley discriminator
 - Ratio detector
 - Quadrature detector





Impedance - Capacity and Inductor

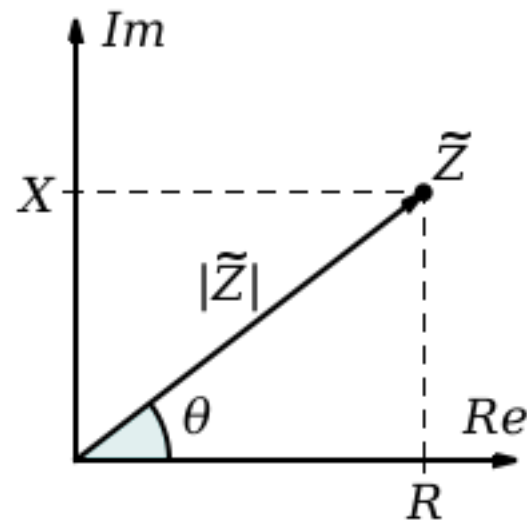

- Complex Impedance (do you recall 'phasor'?)

$$Z = R + jX$$

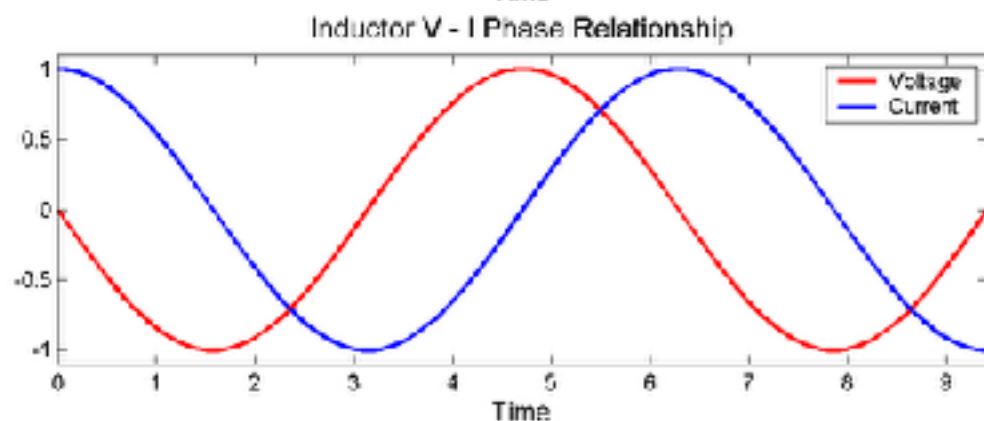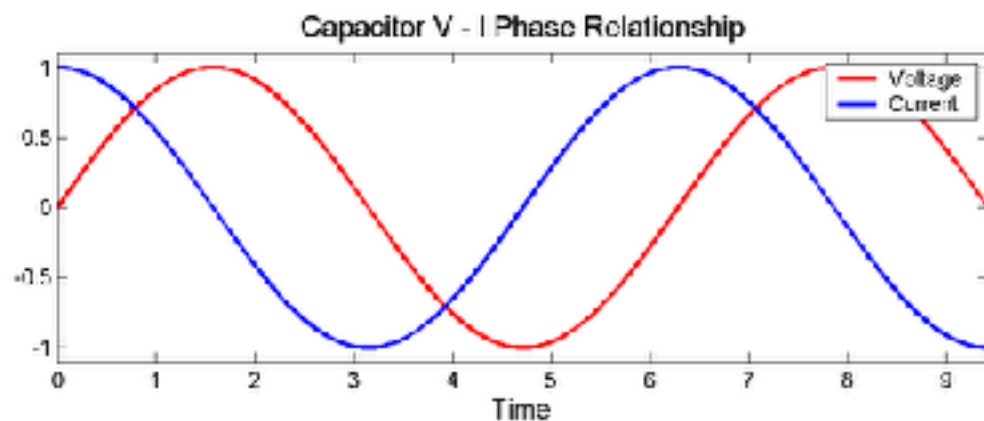

The impedance of an ideal **resistor** is purely real and is referred to as a *resistive impedance*:

$$Z_R = R$$

In this case, the voltage and current waveforms are proportional and in phase.

Ideal **inductors** and **capacitors** have a purely **imaginary reactive impedance**:

the impedance of inductors increases as frequency increases;


$$Z_L = j\omega L$$

the impedance of capacitors decreases as frequency increases;

$$Z_C = \frac{1}{j\omega C}$$



Quadrature Detector

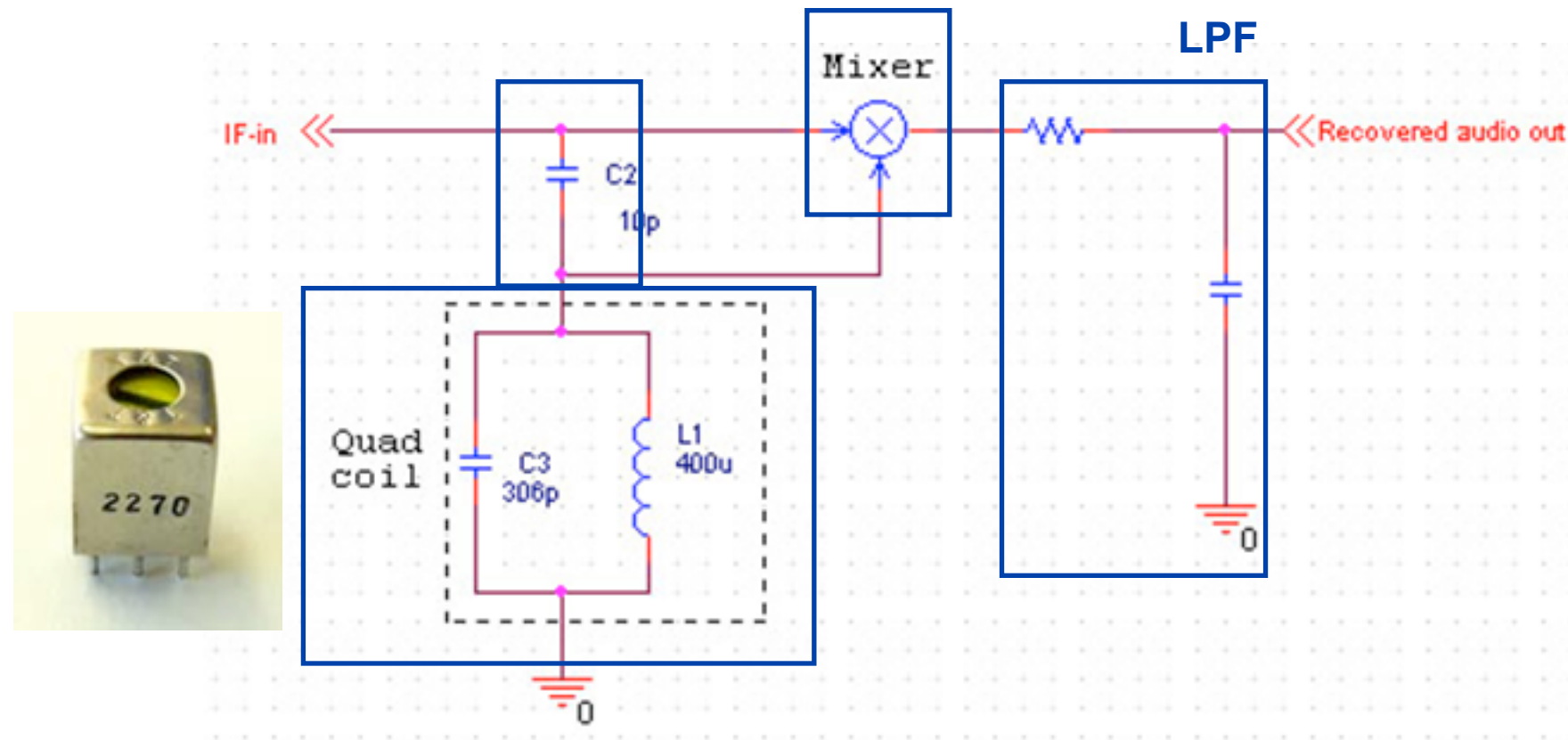



- High-reactance capacitor (C2): produce two signals with 90 degree phase difference (see next slide)
- Phase-shifted signal is then applied to LC-tuned resonant at carrier frequency (L1 and C3)
- Frequency changes will then produce an additional leading or lagging phase shift into the mixer





Recall: Capacitor and Phase

- Flow of electrons “through” capacitor is **directly proportional** to **rate of change** of voltage across capacitor.
- In Math,

$$i = C \frac{dV}{dt}$$

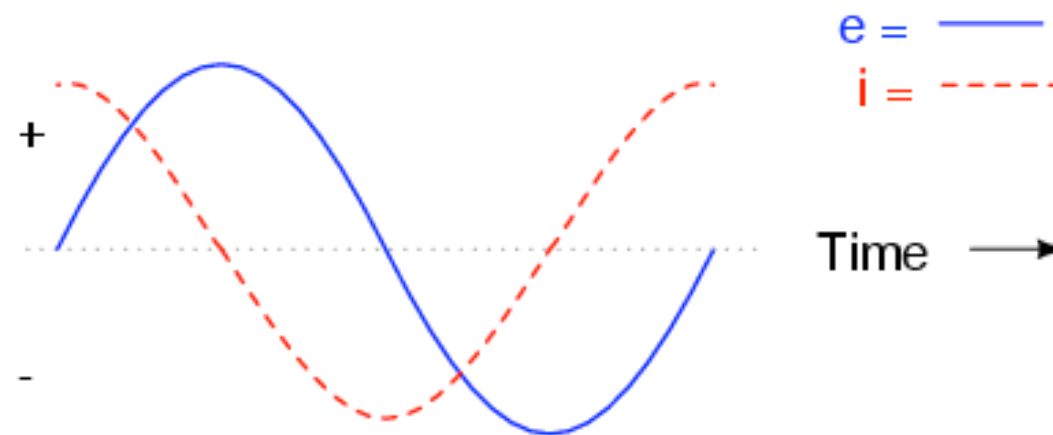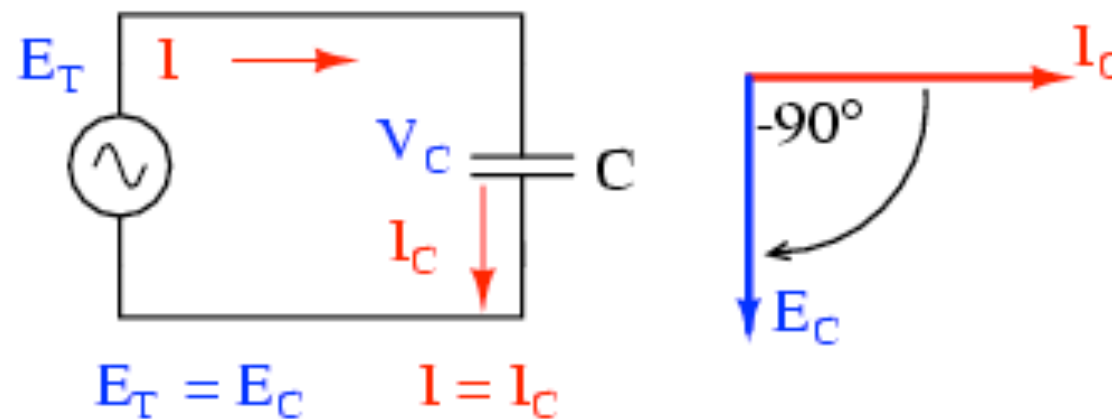

Impedance and Phase of LC tuned Circuit

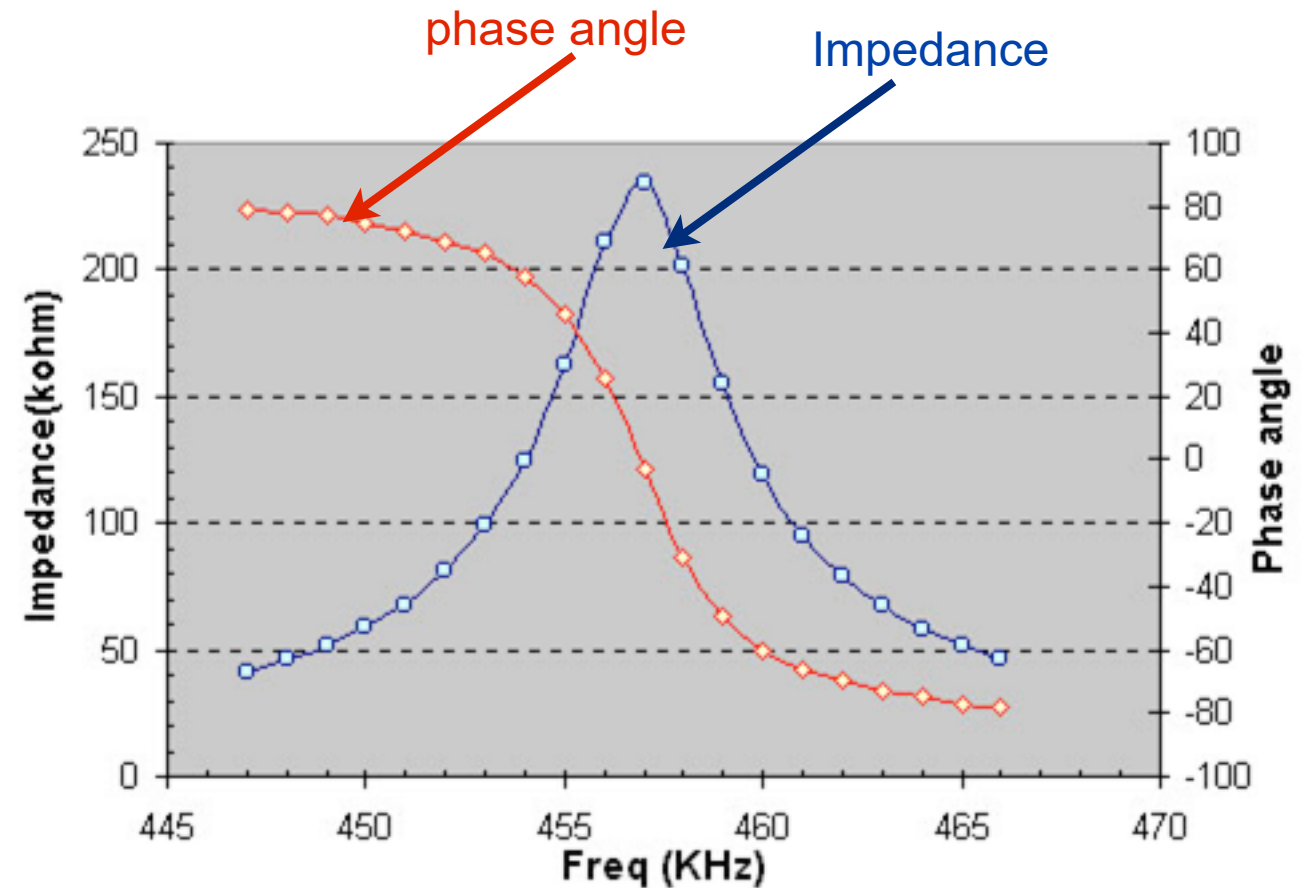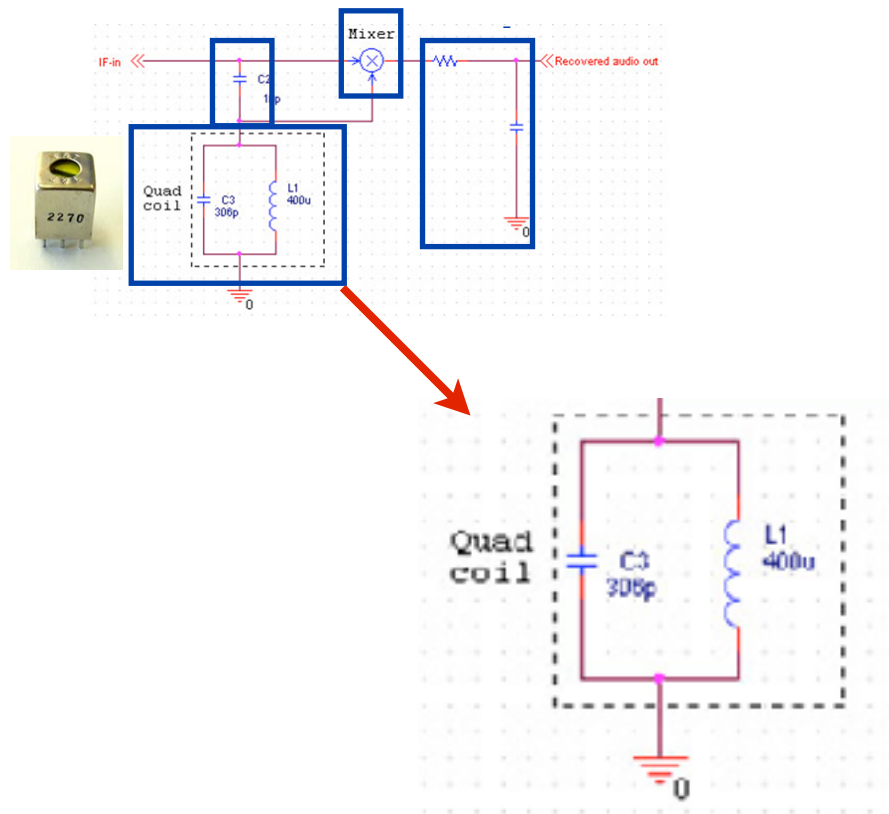


- Facts:
 - Phase (red curve): 0 at resonance
 - Frequency lower than 457KHz: phase positive
 - Frequency higher than 457KHz: phase negative
- In conclusion: If frequency changes, phase will also vary and output voltage (audio signal) too



Property

- **RULE:** multiplication of two periodic signals with same frequency produces **DC voltage** that is directly **proportional to** signal **phase difference**
- Example:
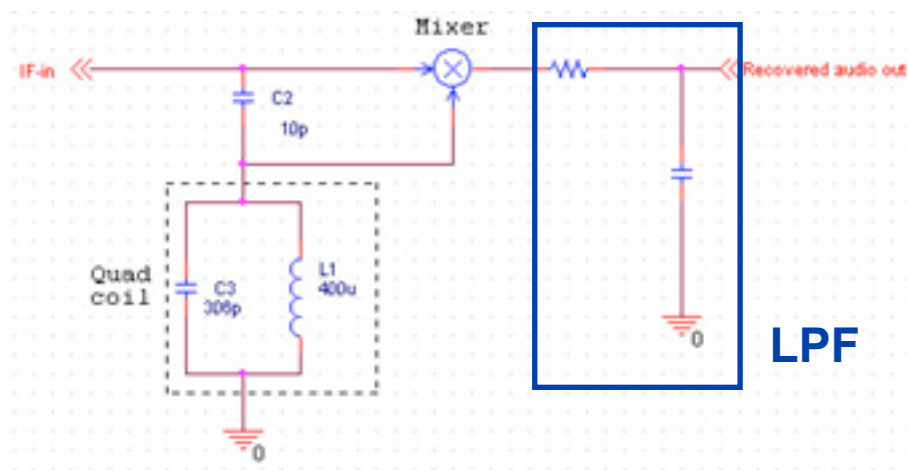
$$\begin{aligned}\sin(x) \sin(90^\circ + x + \theta) &= \sin(x) \cos(x + \theta) \\ &= \frac{1}{2} (\sin(2x + \theta) - \sin(\theta)) \xrightarrow{LPF} -\frac{1}{2} \sin \theta \stackrel{\text{Taylor Expansion}}{\approx} -\frac{1}{2} \theta\end{aligned}$$



- Finally, we can recover signal that is proportion to frequency changes!



Note - Taylor Expansion

- Taylor series of a function $f(x)$ in a is given by

$$f(a) + \frac{f'(a)}{1!}(x-a) + \frac{f''(a)}{2!}(x-a)^2 + \frac{f^{(3)}(a)}{3!}(x-a)^3 + \dots$$

or

$$\sum_{n=0}^{\infty} \frac{f^{(n)}(a)}{n!}(x-a)^n$$

- Examples:

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$



$$\sin x = x - \frac{x^3}{3!} + \frac{x^5}{5!} - \dots$$

$$\cos x = 1 - \frac{x^2}{2!} + \frac{x^4}{4!} - \dots$$




In Experiments,




- In circuit board:

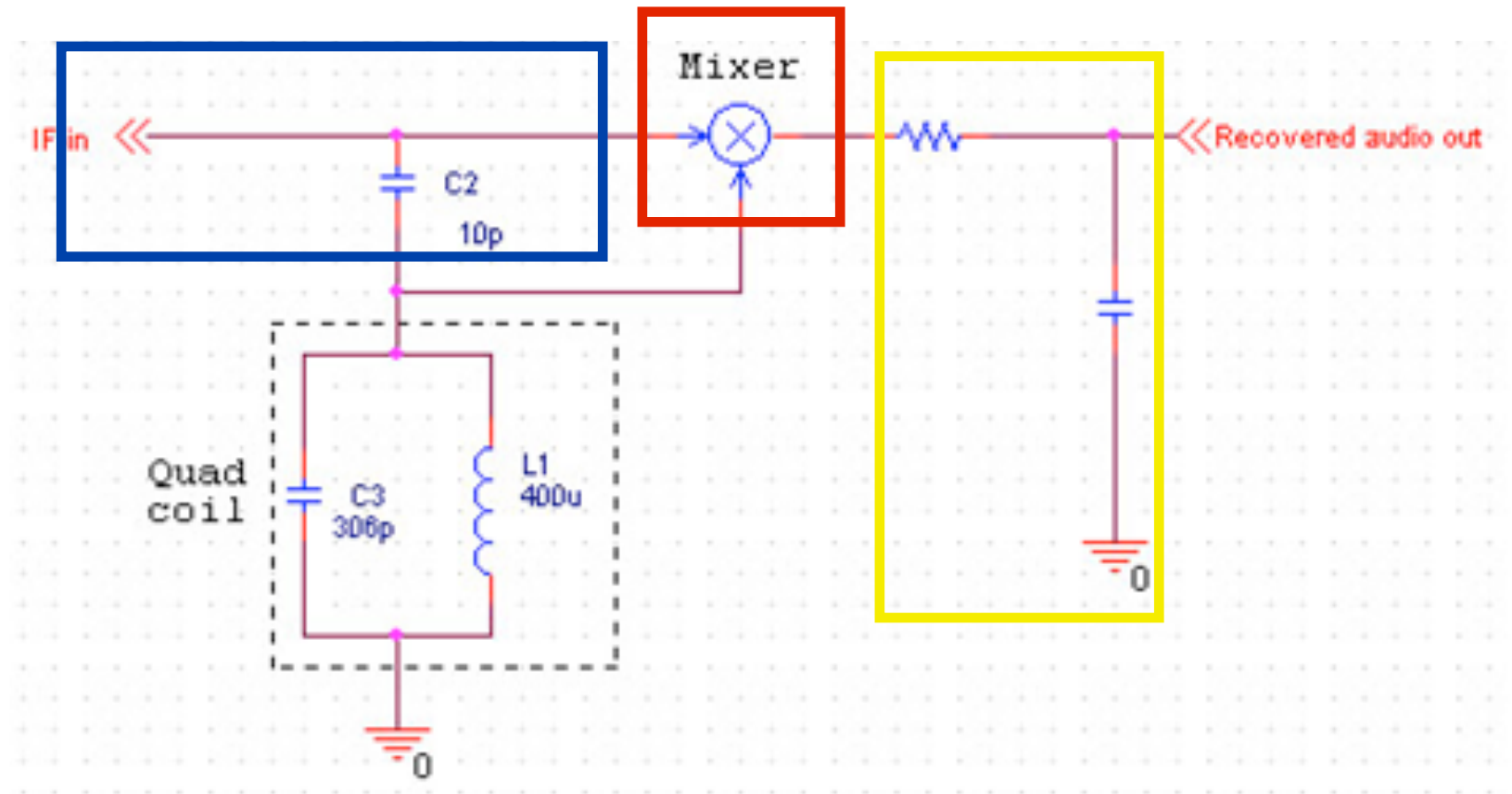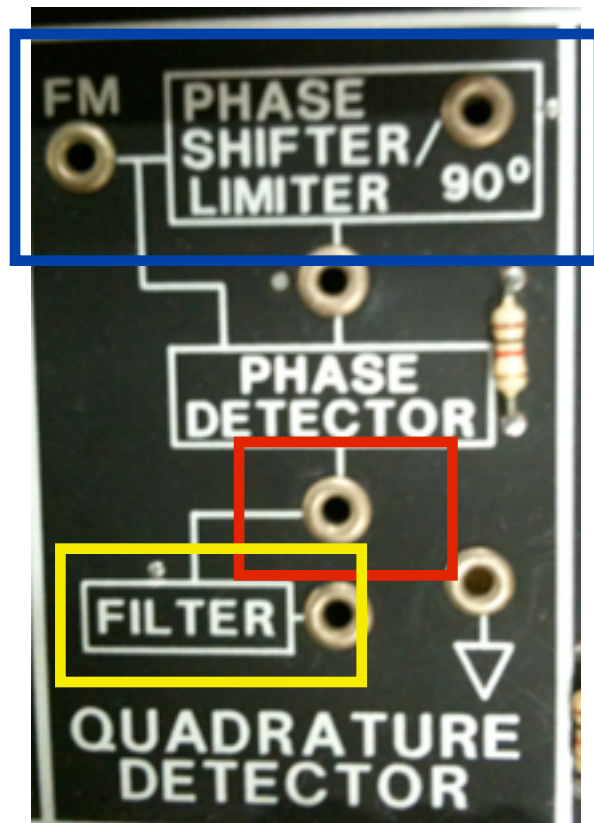


Illustrative Results:

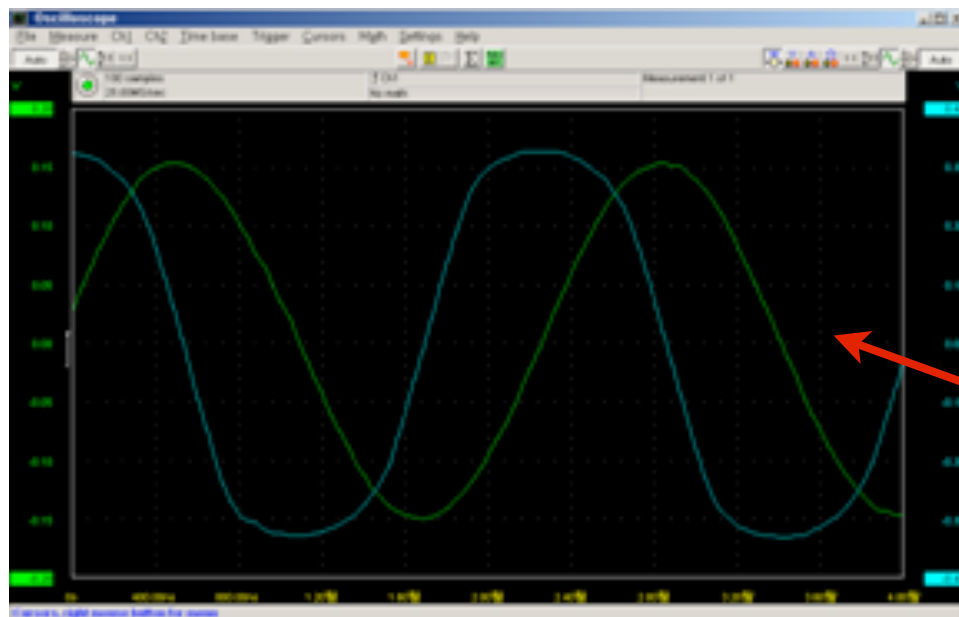

$$\sin(x) \sin(90^\circ + x + \theta)$$

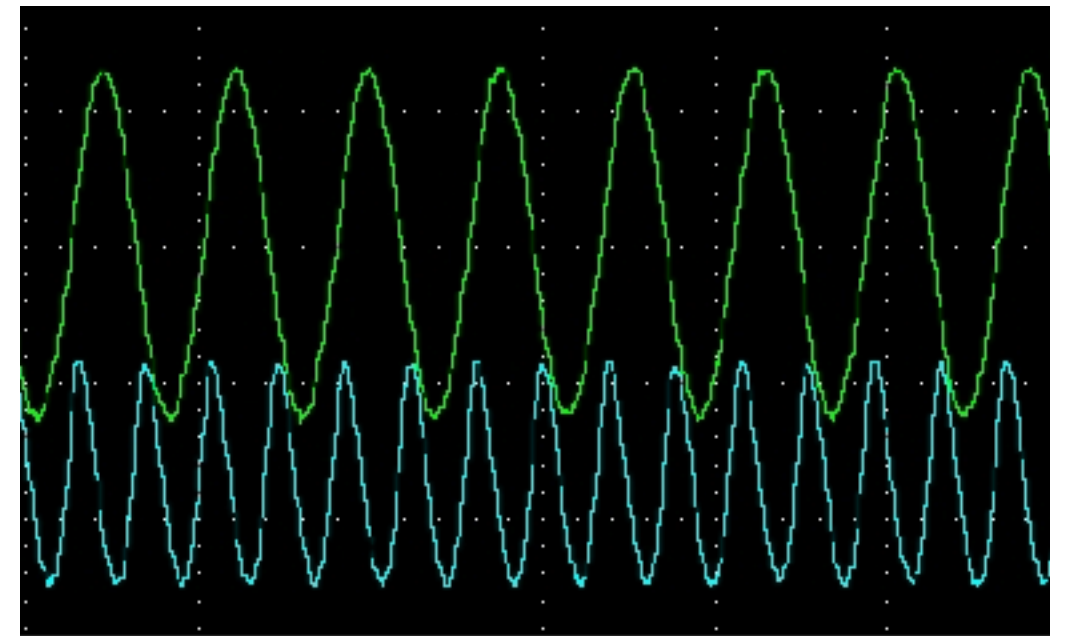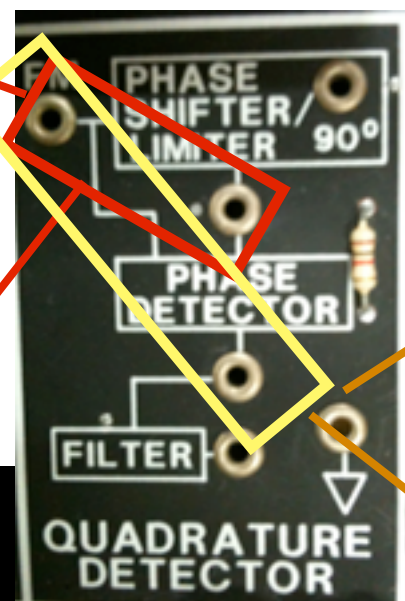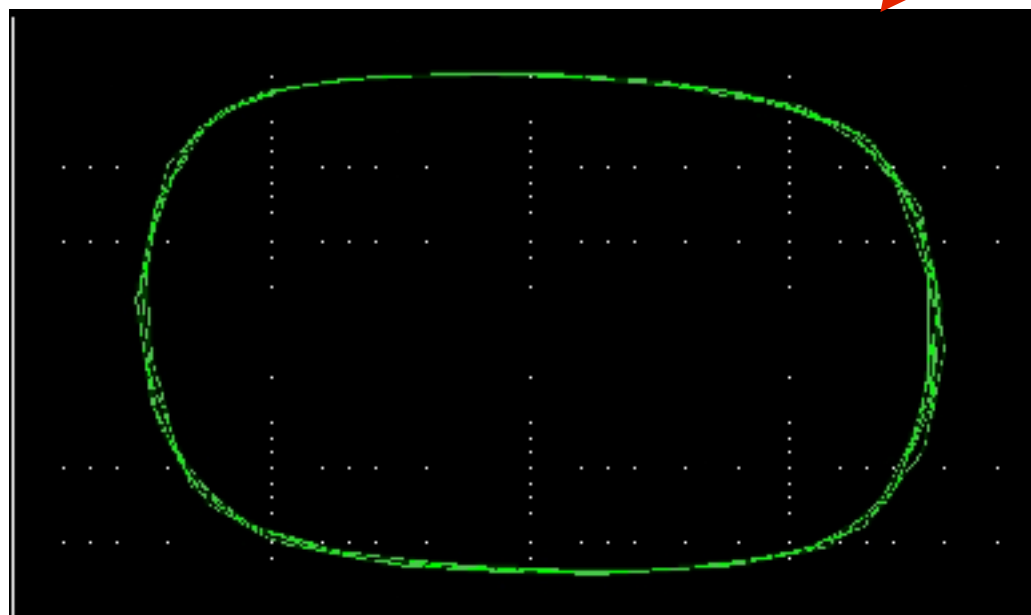
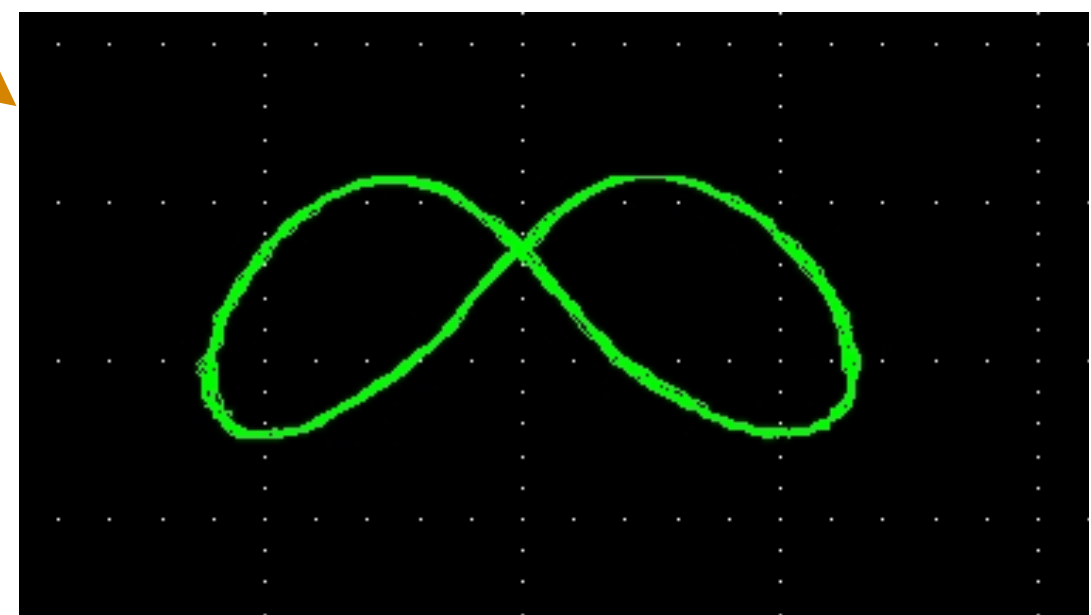
$$\frac{1}{2} (\sin(2x + \theta) - \sin(\theta))$$



Illustrative Results:

